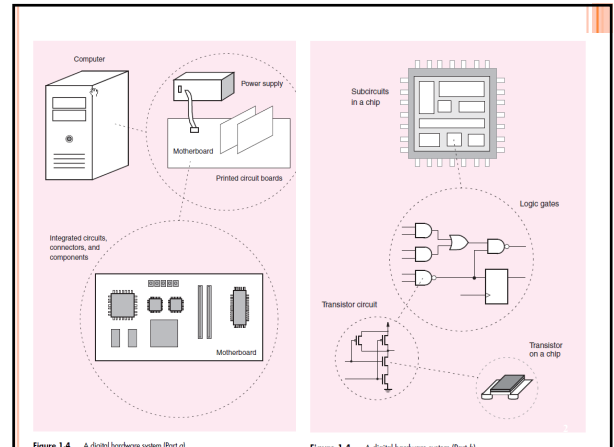


# DIGITAL LOGIC

## Chapter 2: Introduction to logic circuits

Ru Han



### OUTLINE

#### Chapter 2:

#### Introduction to logic circuits


- Logic function and circuits
- Boolean algebra for dealing with logic function
- Logic gates and synthesis of simple circuits
- CAD tools and the Verilog hardware description language
- Minimization of functions and Karnaugh maps

### 2.1 VARIABLES AND FUNCTIONS

**Switch:** Basic element of every digital (computer) system.




(a) Two states of a switch

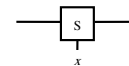

(b) Symbol for a switch

Figure 2.1. A binary switch.


#### Switch application

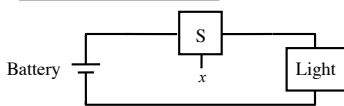

(a) Simple connection to a battery

Light on:  $L=1$   
Light off:  $L=0$

$x=1 \quad L=1$   
 $x=0 \quad L=0$

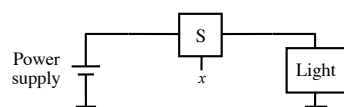


(b) Using a ground connection as the return path

A function of  
the input  
variable  $x$ :  
 $L(x)=x$

Figure 2.2. A light controlled by a switch.

#### Logic Operation: AND

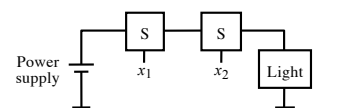

(a) The logical AND function (series connection)

Figure 2.3. Two basic functions.

#### Logic Abstraction:

- Switch  $x_1, x_2$ :  
 $0 = \text{Open}, 1 = \text{Closed}$
- Bulb  $L$ :  
 $0 = \text{Off}, 1 = \text{On}$

$x_1$	$x_2$	$L$
0	0	0
0	1	0
1	0	0
1	1	1

### Logic Operation: AND

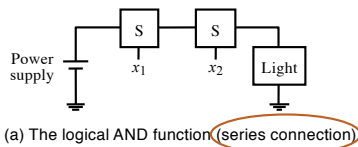


Figure 2.3. Two basic functions.

AND:  $L(x_1, x_2) = x_1 \cdot x_2$

Design a 2-switch light circuit, such that the light is on only when both switches are closed.

### Logic Operation: OR

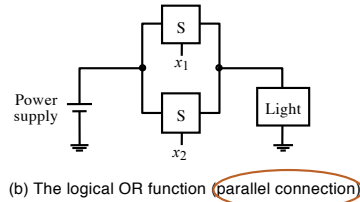


Figure 2.3. Two basic functions.

#### Logic Abstraction:

- Switch  $x_1, x_2$ :  
0 = Open, 1 = Closed
- Bulb L:  
0 = Off, 1 = On

$x_1$	$x_2$	L
0	0	0
0	1	0
1	0	0
1	1	1

### Logic Operation: OR

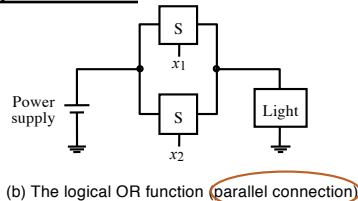


Figure 2.3. Two basic functions.

OR:  $L(x_1, x_2) = x_1 + x_2$

Design a 2-switch light circuit, such that the light is on if either or both switches are closed.

Example: The referee's circuit.

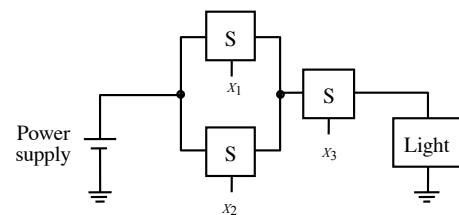


Figure 2.4. A series-parallel connection.

## 2.2 INVERSION

### Logic Operation: NOT

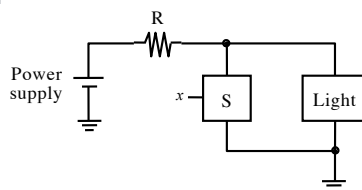


Figure 2.5. An inverting circuit.

#### Logic Abstraction:

- Switch  $x$ :  
0 = Open, 1 = Closed
- Bulb L:  
0 = Off, 1 = On

$x$	L
0	1
1	0

## INVERSION

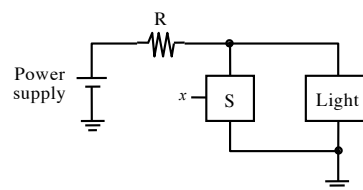


Figure 2.5. An inverting circuit.

NOT:  $L(x) = x' = !x = \neg x$

Design a 1-switch light circuit, such that the light is on only when the switch is open.

## 2.3 TRUTH TABLES

$x_1$	$x_2$	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

AND      OR

Figure 2.6. A truth table for the AND and OR operations.

$x_1$	$x_2$	$x_3$	$x_1 \cdot x_2 \cdot x_3$	$x_1 + x_2 + x_3$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Figure 2.7. Three-input AND and OR operations.

The AND and OR operations can be extended to  $n$  variables.

An AND function of variables  $x_1, x_2, \dots, x_n$  has the value 1 only if all  $n$  variables are equal to 1.

An OR function of variables  $x_1, x_2, \dots, x_n$  has the value 1 if one or more of the variables is equal to 1.

## 2.4 LOGIC GATES AND NETWORKS

### Logic Gates

- Switch Model  $\leftrightarrow$  Logic Gates  $\leftrightarrow$  Physical Devices
- Symbolic Representations
- Functional Descriptions
- Logic Networks
- Logic Design
- Venn Diagrams

### PHYSICAL DEVICES

- Constructed using transistors
- Take one or more electrical input signals, and produce one output signal
- High Voltage (4~5V) = LOGIC 1  
Low Voltage (0~1V) = LOGIC 0  
(Sometime this conversion is reversed)

### SYMBOLIC REPRESENTATIONS

#### (1) AND Gate



- (a)  $\{A, B, X\} \in \{0, 1\}$
- (b) may have  $> 2$  inputs
- (c)  $X = 1$  if and only if **ALL** inputs = 1

### SYMBOLIC REPRESENTATIONS

#### (2) OR Gate



- (a)  $\{A, B, X\} \in \{0, 1\}$
- (b) may have  $> 2$  inputs
- (c)  $Y = 0$  if and only if **ALL** inputs = 0


## SYMBOLIC REPRESENTATIONS

### (3) NOT Gate (Inverter)




- (a)  $\{A, Z\} \in \{0, 1\}$
- (b) 1 input, 1 output
- (c)  $Z = 1$  if and only if  $A = 0$


19

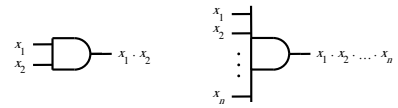

(a) AND gates

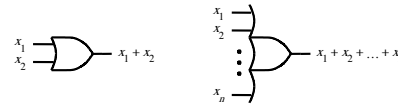

(b) OR gates

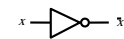

(c) NOT gate

Figure 2.8. The basic gates.

20

## SYMBOLIC REPRESENTATIONS

- Example: 3-input network

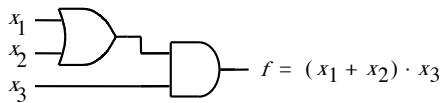


Figure 2.9. The function from Figure 2.4.

21

## FUNCTIONAL DESCRIPTIONS

Design problem:

- Analysis process:

For an existing logic network, it must be possible to determine the function performed by the network.

- Synthesis process:

The reverse task of designing a new network that implements a desired functional behavior.

22

## FUNCTIONAL DESCRIPTIONS

### (1) Logic Function

### (2) Truth Table

- Table that lists all possible combinations of inputs, and the corresponding output.
- Example, 3-input AND gate.



A	B	C	X

23

## FUNCTIONAL DESCRIPTIONS

### (1) Logic Function

### (2) Truth Table

- Table that lists all possible combinations of inputs, and the corresponding output.
- Example, 3-input AND gate.



A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

24

## FUNCTIONAL DESCRIPTIONS

### (3) Timing Diagram


- Draw waveforms to show inputs and outputs as functions of time.
- Create waveforms so that all possible input combinations are shown, then determine output waveform.
- Gives all information in truth table PLUS implementation details such as propagation delay.

25

## FUNCTIONAL DESCRIPTIONS

### (3) Timing Diagram

- Example, 3-input AND gate

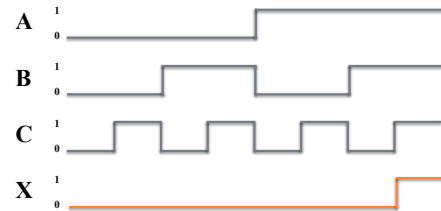

26


## LOGIC NETWORK

- Any logic function with any number of input signals can be realized as a network of AND, OR, and NOT gates.
- We can use truth tables and timing diagrams to analyze network.
  - Provide columns in truth table, or waveforms in timing diagram for all inputs, outputs and intermediate signals.
- Note: We Will Use Logic Network Or Logic Circuit Interchangeably

27

## LOGIC NETWORK

- Example: 2-input network

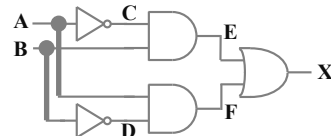


### (a) Algebraic Evaluation

$$\begin{aligned} C &= \bar{A} \\ D &= \bar{B} \\ E &= C \bullet B = \bar{A} \bullet B \\ F &= A \bullet D = A \bullet \bar{B} \\ X &= E + F = (A \bullet B) + (A \bullet \bar{B}) \end{aligned}$$

28

## LOGIC NETWORK

- Example: 2-input network

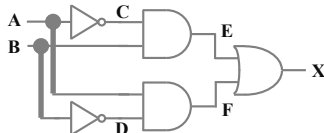


### (B) Truth Table

A	B	C	D	E	F	X
0	0					
0	1					
1	0					
1	1					

29

## LOGIC NETWORK

- Example: 2-input network

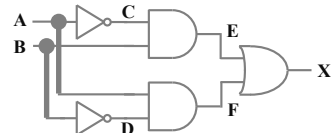

### (B) Truth Table

A	B	C	D	E	F	X
0	0					
0	1					
1	0					
1	1					



Note: This type of network is known as Exclusive-OR (XOR)



30

## LOGIC NETWORK

### (C) Timing Diagram

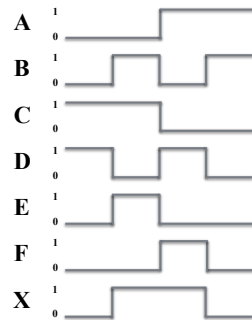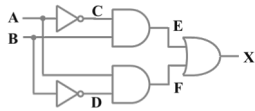

31


## FUNCTIONAL EQUIVALENT NETWORK

- For any logic function, there are **many different networks** that could be used to implement the function.
- If two networks have the same output column in their truth tables, then they are **functional equivalent**.

32

## FUNCTIONAL EQUIVALENT NETWORK

- Example: 2-input network

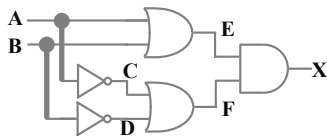


### (a) Algebraic Evaluation

33

## FUNCTIONAL EQUIVALENT NETWORK

- Example: 2-input network

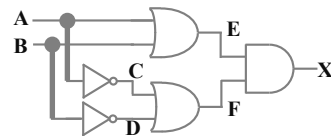


### (a) Algebraic Evaluation

$$\begin{aligned} C &= \bar{A} \\ D &= \bar{B} \\ E &= A + B \\ F &= C + D = \bar{A} + \bar{B} \\ X &= E \cdot F = (A + B) \cdot (\bar{A} + \bar{B}) \end{aligned}$$

34

## FUNCTIONAL EQUIVALENT NETWORK

- Example: 2-input network

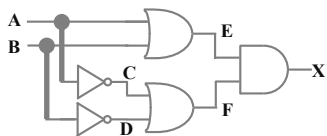


### (B) Truth Table

35

## FUNCTIONAL EQUIVALENT NETWORK

- Example: 2-input network

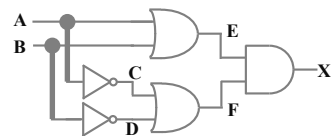


### (B) Truth Table

A	B	C	D	E	F	X
0	0	1	1	0	1	0
0	1	1	0	1	1	1
1	0	0	1	1	1	1
1	1	0	0	1	0	0

It is also an XOR network

36




## FUNCTIONAL EQUIVALENT NETWORK

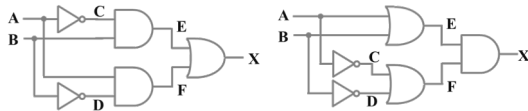

- The two logic networks are used to implement the same function – XOR gate.
- They are functional equivalent networks.

37

## FUNCTIONAL EQUIVALENT NETWORK

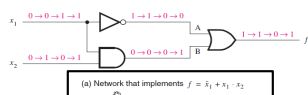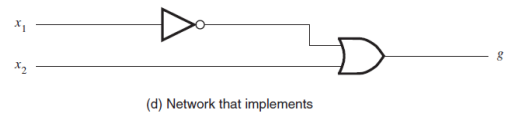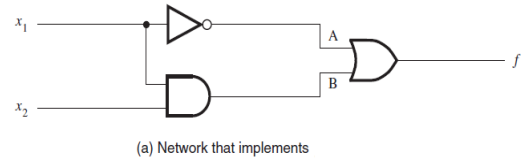

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	0
0	1	0
1	0	1
1	1	1

(b) Truth table

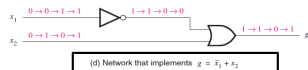
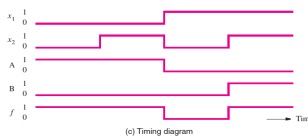


Figure 2.10. An example of logic networks.

39

SO:

- More than one logic functions based on One Truth Table
- They are functional equivalent networks
- Is there one network which is the best for cost among them ?
- **Boolean Algebra Will Give You The Answer**

40

## CONCLUSION

- Logic variable and functions
- Understand the Truth Table
- Truth table/timing diagram/ Logic function
- XOR
- Text Reading: Chapter: 2.1 ~ 2.4, page22~33
- Assignment: Page 111: 2.8

41

## 2.5 BOOLEAN ALGEBRA

### Boolean Algebra

- Huntington's Postulates
- Proofs
- Basic Theorems
- Operator Precedence

42

## BOOLEAN ALGEBRA

In 1845, George Boole introduced a systematic treatment of logic now called **Boolean algebra**. Logical statements are built up from:

- **Variables:**  $a, x$ , etc. Variables can be used to represent propositions (statements that are either true or false) or signals in digital circuits (voltages that are either high or low, representing 0 or 1).
- **Operators:** The two operators  $(+, \bullet)$  are used to combine variables to produce more complex statements or logic functions. These operators must satisfy certain properties.

The most well-known form of Boolean algebra is a two-valued system, in which all variables take values on the set  $\{0, 1\}$  and the operators  $(+, \bullet)$  correspond to (OR, AND) respectively.

43

**Huntington's Postulates:** In 1904, E. V. Huntington defined Boolean algebra by providing 6 postulates that must be satisfied.

- **Closure** with respect to the operators:  
any logical operation yields a value in the set  $\{0, 1\}$ .
- **Identity** elements with respect to the operators:  
 $x + 0 = x$                        $x \bullet 1 = x$
- **Commutativity** with respect to the operators:  
 $x + y = y + x$                        $x \bullet y = y \bullet x$
- **Distributivity:**  
 $x \bullet (y + z) = (x \bullet y) + (x \bullet z)$                        $x + (y \bullet z) = (x + y) \bullet (x + z)$
- **Complements** exist for all the elements:  
 $x + x' = 1$                        $x \bullet x' = 0$
- **Distinct elements:**  
 $0 \neq 1$

44

- In 1938, Claude Shannon showed that a two-valued Boolean Algebra, called **switching algebra**, could be used to describe *digital circuits*.

- Two elements:  $\{0, 1\}$
- Two binary operators:  $+$  (OR),  $\bullet$  (AND)
- One unary operator: the complement  $'$  ( $\neg$ )

$x$	$y$	$x + y$	$x$	$y$	$x \bullet y$	$x$	$x'$
0	0	0	0	0	0	0	1
0	1	1	0	1	0	1	0
1	0	1	1	0	0		
1	1	1	1	1	1		

45

## IS THIS REALLY A BOOLEAN ALGEBRA? DOES IT SATISFY HUNTINGTON'S POSTULATES?

- **Closure** with respect to  $+, \bullet$ :  
Yes, both operations produce 0 or 1 for all input combinations.
- **Identity** elements with respect to  $+, \bullet$ :  
Yes, from truth tables,  $x + 0 = x$ ,  $x \bullet 1 = x$ .
- **Commutativity** with respect to  $+, \bullet$ :  
Yes, if  $x$  and  $y$  columns are swapped, results are unchanged.

$x$	$y$	$x + y$	$x$	$y$	$x \bullet y$	$x$	$x'$
0	0	0	0	0	0	0	1
0	1	1	0	1	0	1	0
1	0	1	1	0	0		
1	1	1	1	1	1		

46

## IS THIS REALLY A BOOLEAN ALGEBRA? DOES IT SATISFY HUNTINGTON'S POSTULATES?

- **Distributivity:**  
Yes (proof to follow).
- **Complements** exist for all the elements:  
Yes,  $0' = 1$ ,  $1' = 0$ .
- **Distinct Elements:**  
Yes, by definition:  $0 \neq 1$ .

$x$	$y$	$x + y$	$x$	$y$	$x \bullet y$	$x$	$x'$
0	0	0	0	0	0	0	1
0	1	1	0	1	0	1	0
1	0	1	1	0	0		
1	1	1	1	1	1		

47

## IS THIS REALLY A BOOLEAN ALGEBRA? DOES IT SATISFY HUNTINGTON'S POSTULATES?

- **Closure** with respect to  $+, \bullet$ :  
Yes, both operations produce 0 or 1 for all input combinations.
- **Identity** elements with respect to  $+, \bullet$ :  
Yes, from truth tables,  $x + 0 = x$ ,  $x \bullet 1 = x$ .
- **Commutativity** with respect to  $+, \bullet$ :  
Yes, if  $x$  and  $y$  columns are swapped, results are unchanged.
- **Distributivity:**  
Yes (proof to follow).
- **Complements** exist for all the elements:  
Yes,  $0' = 1$ ,  $1' = 0$ .
- **Distinct Elements:**  
Yes, by definition:  $0 \neq 1$ .

Note: In this book,  
it is called **Axioms**  
On pages:33

48



## PROOFS: WHAT ARE THEY?

Proofs are a tool for establishing new results or **theorems** in Boolean algebra. The kinds of things we need to prove usually fall into one of several categories.

- Prove that two logical expressions are equivalent.
- Prove that two logic networks are functionally equivalent.
- Prove that one logical expression is the complement of another.

49

## OK, SO PROVE IT! HMMM, HOW DO WE DO THAT?

Here are four ways to prove that two expressions are equivalent.

- **Perfect Induction**: show that the two expressions have identical truth tables.  
If there are  $n$  input variables, this requires  $2^n$  input combinations. This is a bad idea if there are more than 3 or 4 variables.
- **Axiomatic Proof**: apply Huntington's postulates (or other theorems that have already been proven) to the expressions, until the two expressions are identical.
- **Duality Principle**: every theorem in Boolean algebra remains valid if we interchange all AND's and OR's, and interchange all 0's and 1's.
- **Proof by contradiction**: assume that the hypothesis is *false* and then prove that the resulting equation can never be true.

50

## DUALITY

- Given a logic expression, its dual can be obtained by
  1. Replace all + with  $\cdot$  and vice versa
  2. Replace all 0 with 1 and vice versa

Pages: 34

- Understand the importance of the duality



## HOW TO UNDERSTAND DUALITY PRINCIPLE

The duality principle ensures that "if we exchange *every* symbol by its dual in a formula, we get the *dual* result".

Examples:

- $0 \cdot 1 = 0$  is a true statement asserting that "false and true evaluates to false"  
 $1 + 0 = 1$  is its dual: it is a true statement asserting that "true or false evaluates true."
- $1 \cdot 1 = 1$  is a true statement asserting that "true and true evaluates to true".  
 $0 + 0 = 0$  is its dual: it is a true statement asserting, correctly, that "false or false evaluates to false".

52

## PROOF OF DISTRIBUTIVITY OF $\cdot$ OVER $+$ , BY PERFECT INDUCTION.

$$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

$x$	$y$	$z$	$y + z$	$x \cdot (y + z)$	$x \cdot y$	$x \cdot z$	$(x \cdot y) + (x \cdot z)$
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

53

## PROOF OF DISTRIBUTIVITY OF $\cdot$ OVER $+$ , BY PERFECT INDUCTION.

$$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

$x$	$y$	$z$	$y + z$	$x \cdot (y + z)$	$x \cdot y$	$x \cdot z$	$(x \cdot y) + (x \cdot z)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

54

**PROOF OF DISTRIBUTIVITY OF + OVER •, BY PERFECT INDUCTION.**

$$x + (y \bullet z) = (x + y) \bullet (x + z)$$

x	y	z	y • z	x + (y • z)	x + y	x + z	(x + y) • (x + z)
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

55

**PROOF OF DISTRIBUTIVITY OF + OVER •, BY PERFECT INDUCTION.**

$$x + (y \bullet z) = (x + y) \bullet (x + z)$$

x	y	z	y • z	x + (y • z)	x + y	x + z	(x + y) • (x + z)
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

56

**OK, WHERE ARE WE SO FAR?**

- So far, we have only shown (through 1 rigorous proof and several less formal arguments) that Huntington's postulates are satisfied. Therefore, the two valued system with the operations (•, +) as defined above is a Boolean algebra.

**Why do we care?**

- Armed with these 6 postulates, we can now go on to establish other theorems that will help us analyze logic circuits.

57

**BASIC THEOREMS**

These theorems can be verified by examining the truth tables for {+, •, ' }.

• **Theorem 1: Idempotency**

- a)  $x + x = x$
- b)  $x \bullet x = x$

x	x + x	x • x
0	0	0
1	1	1

• **Theorem 2: Tautology & Contradiction**

- a)  $x + 1 = 1$
- b)  $x \bullet 0 = 0$

x	x + 1	x • 0
0	1	0
1	1	0

• **Theorem 3: Involution**

- (x')' = x

x	x'	(x')'
0	1	0
1	0	1

58

**BASIC THEOREMS**

• **Theorem 4: Associativity**

- a)  $(x + y) + z = x + (y + z)$

x	y	z	(x + y)	(y + z)	(x + y) + z	x + (y + z)
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

59

**BASIC THEOREMS**

• **Theorem 4: Associativity**

- a)  $(x + y) + z = x + (y + z)$

x	y	z	(x + y)	(y + z)	(x + y) + z	x + (y + z)
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	0	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

60

## BASIC THEOREMS

### ○ Theorem 4: *Associativity*

- a)  $(x + y) + z = x + (y + z)$   
 b)  $(x \bullet y) \bullet z = x \bullet (y \bullet z)$

$x$	$y$	$z$	$(x \bullet y)$	$(y \bullet z)$	$(x \bullet y) \bullet z$	$x \bullet (y \bullet z)$
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

61

## BASIC THEOREMS

### ○ Theorem 4: *Associativity*

- a)  $(x + y) + z = x + (y + z)$   
 b)  $(x \bullet y) \bullet z = x \bullet (y \bullet z)$

$x$	$y$	$z$	$(x \bullet y)$	$(y \bullet z)$	$(x \bullet y) \bullet z$	$x \bullet (y \bullet z)$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	1	0	0	0
1	1	1	1	1	1	1

62

## THEOREM 5: DEMORGAN'S LAW

- (a)  $(x + y)' = x' \bullet y'$

**Proof:** by Perfect Induction.

$x$	$y$	$(x + y)$	$(x + y)'$	$x'$	$y'$	$x' \bullet y'$
0	0					
0	1					
1	0					
1	1					

63

## THEOREM 5: DEMORGAN'S LAW

- (a)  $(x + y)' = x' \bullet y'$

**Proof:** by Perfect Induction.

$x$	$y$	$(x + y)$	$(x + y)'$	$x'$	$y'$	$x' \bullet y'$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

- (b)  $(x \bullet y)' = x' + y'$

**Proof:** apply the duality principle to the expression in part (a). If we interchange all  $\bullet$  and  $+$  operators, we obtain the expression in part (b).

64

## THEOREM 6: ABSORPTION

- (a)  $x + (x \bullet y) = x$

**Axiomatic Proof:**

$$\begin{aligned}
 x + (x \bullet y) &= (x \bullet 1) + (x \bullet y) && \text{by } x \bullet 1 = x \\
 &= x \bullet (1 + y) && \text{by distributivity} \\
 &= x \bullet (y + 1) && \text{by commutativity} \\
 &= x \bullet 1 && \text{by } x + 1 = 1 \\
 &= x && \text{by } x \bullet 1 = x
 \end{aligned}$$

- (b)  $x \bullet (x + y) = x$

**Proof:** apply the duality principle to the expression in part (a). If we interchange all  $\bullet$  and  $+$  operators, we obtain the expression in part (b).

65

## TWO MORE THEOREMS

### ○ Theorem 7: *Common Identities*

- a)  $x + (x' \bullet y) = x + y$   
 b)  $x \bullet (x' + y) = x \bullet y$

### ○ Theorem 8: *Consensus*

- a)  $(x \bullet y) + (y \bullet z) + (x' \bullet z) = (x \bullet y) + (x' \bullet z)$   
 b)  $(x + y) \bullet (y + z) \bullet (x' + z) = (x + y) \bullet (x' + z)$

- Try to prove these theorems on your own.  
 ○ Note that each pair of equations are related through the duality principle.

66

SO NOW WE HAVE ALL THESE THEOREMS. WHAT GOOD ARE THEY?

**Example 1:** Find the complement of the logical function  $f$ .

$$f = \bar{x} \bullet (\bar{y} + \bar{z}) \bullet (x + y + \bar{z})$$

**Solution:** by repeated application of DeMorgan's Law.

$$\begin{aligned}\bar{f} &= \overline{\bar{x} \bullet (\bar{y} + \bar{z}) \bullet (x + y + \bar{z})} \\ &= \overline{\bar{x}} \bullet \overline{(\bar{y} + \bar{z})} \bullet \overline{(x + y + \bar{z})} \\ &= \bar{\bar{x}} \bullet \overline{(\bar{y} + \bar{z})} \bullet \overline{(x + y + \bar{z})} \\ &= x \bullet (y \bullet z) \bullet (\bar{x} \bullet \bar{y} \bullet \bar{z})\end{aligned}$$

67

SO NOW WE HAVE ALL THESE THEOREMS. WHAT GOOD ARE THEY?

**Example 2:** Simplify the previous expression.

$$\bar{f} = x + (y \bullet z) + (\bar{x} \bullet \bar{y} \bullet \bar{z})$$

**Solution:** by algebraic manipulation.  
Apply the theorems of Boolean algebra.

$$\begin{aligned}\bar{f} &= x + (\bar{x} \bullet \bar{y} \bullet \bar{z}) + (y \bullet z) && \text{by Commutativity} \\ &= x + (\bar{y} \bullet \bar{z}) + (y \bullet z) && \text{by Theorem 7a} \\ &= x + (\bar{y} + y) \bullet z && \text{by Distributivity} \\ &= x + 1 \bullet z && \text{by Postulate 5a} \\ &= x + z && \text{by Postulate 2b}\end{aligned}$$

68

## MORE EXAMPLES

Equivalent Expression	Justification
$\bar{x}y\bar{z} + \bar{x}yz + x\bar{y}\bar{z} + xy\bar{z} + xyz$	Original Expression
$(\bar{x}y\bar{z} + \bar{x}yz) + (x\bar{y}\bar{z} + xy\bar{z}) + (xyz + xy\bar{z})$	Idempotency
$\bar{x}y(\bar{z} + z) + x\bar{z}(\bar{y} + y) + xy(\bar{z} + z)$	Distributivity
$\bar{x}y(1) + x\bar{z}(1) + xy(1)$	Complement
$\bar{x}y + x\bar{z} + xy$	Identity for AND
$y(\bar{x} + x) + x\bar{z}$	Distributivity
$y(1) + x\bar{z}$	Complement
$y + x\bar{z}$	Identity for AND

69

## EXAMPLE ON PAGES:36

- Example 2.3
- Example 2.4

## PRECEDENCE OF BOOLEAN OPERATORS

- To avoid confusion or incorrect evaluation, the operators in Boolean expressions are applied according to the following order of precedence:

- Expressions in parentheses:  $()$
- NOT:  $'$
- AND:  $\bullet$
- OR:  $+$

- Also, it is conventional to omit the  $\bullet$  symbol for AND where convenient. As a result, many Boolean expressions can be written in a compact form, often eliminating extraneous parentheses.

$$\begin{aligned}(\bar{x} \bullet \bar{y}) &\Leftrightarrow \bar{x}\bar{y} \\ x \bullet (y + z) &\Leftrightarrow x(y + z) \\ (\bar{x} \bullet z) + (\bar{y} \bullet \bar{z}) &\Leftrightarrow \bar{x}z + \bar{y}\bar{z}\end{aligned}$$

71

## REFERENCE SHEET: POSTULATES AND THEOREMS

- Postulate 1: Closure
- Postulate 2: Identity
  - $x + 0 = x$
  - $x \bullet 1 = x$
- Postulate 3: Commutativity
  - $x + y = y + x$
  - $xy = yx$
- Postulate 4: Distributivity
  - $x(y + z) = xy + xz$
  - $x + yz = (x + y)(x + z)$
- Postulate 5: Complement
  - $x + x' = 1$
  - $x \bullet x' = 0$
- Theorem 1: Idempotency
  - $x + x = x$
  - $x \bullet x = x$
- Theorem 2: Tautology and Contradiction
  - $x + 1 = 1$
  - $x \bullet 0 = 0$
- Theorem 3: Involution
  - $(x')' = x$
- Theorem 4: Associativity
  - $x + (y + z) = (x + y) + z$
  - $x(yz) = (xy)z$
- Theorem 5: DeMorgan's Law
  - $(x + y)' = x'y'$
  - $(xy)' = x' + y'$
- Theorem 6: Absorption
  - $x + xy = x$
  - $x(x + y) = x$
- Theorem 7: Common Identities
  - $x + x'y = x + y$
  - $x(x' + y) = xy$
- Theorem 8: Consensus
  - $xy + yz + x'z = xy + x'z$
  - $(x + y)(y + z)(x' + z) = (x + y)(x' + z)$

Notice: 1. Precedence : " $()$ " > "<math>'</math>" > "<math>\bullet</math>" > "<math>+</math>"  
2.  $A \bullet B$  can be written as  $AB$ .

72

## VENN DIAGRAMS

- A graphical technique to illustrate logic functions
- **Large rectangle** to represent all possible input combinations
- **Overlapping bubbles** to represent each input variable
- Represent logical function by **sharing regions** where the function is equal to 1

73


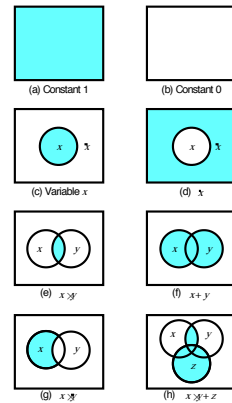


Figure 2.14. The Venn diagram representation.

74

## VENN DIAGRAMS

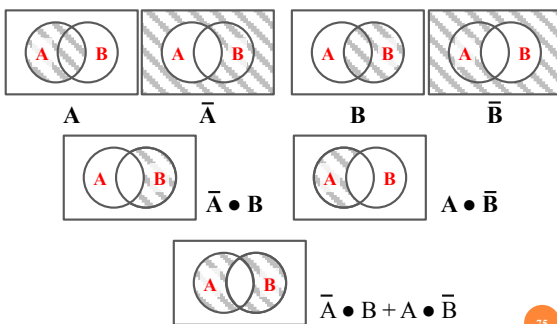- Example:  $X = \bar{A} \bullet B + A \bullet \bar{B}$



75

## CONCLUSION

- Axioms of Boolean algebra
- Duality
- Properties (7 kinds and includes 16 identities )
- Can use the Properties freely to simplify or prove or explain logic expressions
- Textbook Reading: Chapter 2.5, Pages:33-43
- Assignment: Page 111: 2.2 , 2.3 and 2.7

▶

76