

# DIGITAL LOGIC

## Chapter 2: Introduction to logic circuits

Ru Han

### 2.6 SYNTHESIS USING AND, OR, AND NOT GATES

Given a set of specifications, design a logic network to meet them. In this part of Chapter 2, we will explore systematic techniques for doing this.

A simple example:

Design a circuit: The function of the circuit is to continuously monitor the state of the switches.

If the state of the switches ( $x_1, x_2$ ) are in states (0,0), (0,1), (1,1), the output are 1.

If the state of the switches is (1,0), the output should be 0.

### LOGIC DESIGN 1

The truth table:

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

Figure 2.19. A function to be synthesized.

- Our aim: to derive a logic expression which are equal to the truth table in function.
- How ?
- Why ?

### LOGIC DESIGN 1

The truth table:

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1


Figure 2.19. A function to be synthesized.

- Two ways:
  - From AND logic.
  - From OR logic.
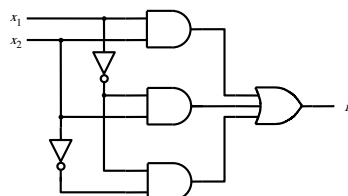
### LOGIC DESIGN 1

**Design 1:** *From the view of AND logic*

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$




(a) Canonical sum-of-products

Figure 2.20. Two implementations of the function in Figure 2.19.

### LOGIC DESIGN 1

**Design 2:** *From the view of OR logic*

$$f(x_1, x_2) = x_2 + \bar{x}_1$$

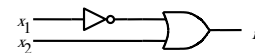

(b) Minimal-cost realization

Figure 2.20. Two implementations of the function in Figure 2.19.

As the truth table is same, so

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 = x_2 + \bar{x}_1$$

- Can you prove the identity?
- Can you get some clues to design the logic circuits based on the truth table?

## A STRAIGHTFORWARD IMPLEMENTATION OF A TRUTH TABLE FROM AND LOGIC

- 1: choose the rows in which the output is 1
- 2: generate the product term for each row.
  - What is the Product term?
  - Product term: Combine all input Variables by AND , each input variable just appears one time in either original form or complement form.
  - In the input valuation, If current input value is 1, then original form  $x_i$  is entered into Product term, else  $\bar{x}_i$  is used.
- 3: OR all the Product terms to realize the desired function

7

## FURTHERMORE :

- There are many different networks to realize a given function.
- At least there is two ways, one based on the AND strategy and another based on the OR strategy.
- Boolean Algebraic manipulation can prove that they are equal in function.
- Boolean Algebraic manipulation can help us to find the simplified and lower-cost networks.

### Synthesis:

The process whereby we begin with a description of the desired functional behavior and then generate a circuit that realizes this behavior is called *synthesis*.

8

## LOGIC DESIGN 2

### Truth Table

$x$	$y$	$z$	name	$f$
0	0	0	$M_0$	
0	0	1	$M_1$	
0	1	0	$M_2$	
0	1	1	$M_3$	
1	0	0	$M_4$	
1	0	1	$M_5$	
1	1	0	$M_6$	
1	1	1	$M_7$	

**Note:**  $f = 1$  if  $x = 0, y = z = 1$   
or  $x = y = z = 1$

9


## LOGIC DESIGN 2

### Design 1:

Let  $M_3 = \bar{x} \cdot y \cdot z = 1$  only when  $x = 0, y = z = 1$

Let  $M_7 = x \cdot y \cdot z = 1$  only when  $x = y = z = 1$

Then  $f = M_3 + M_7$

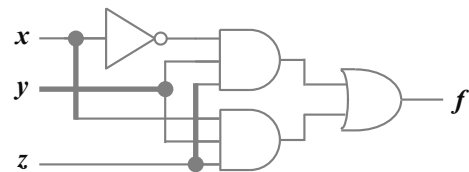

10

## LOGIC DESIGN 2

### Design 2:

Further note:  $f = 1$  if  $y = z = 1$   
independent of  $x$  value


→  $f = y \cdot z$




11

## LOGIC DESIGN

### Design 1:

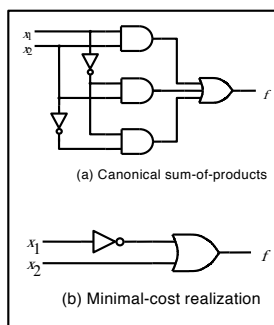

### Design 2:

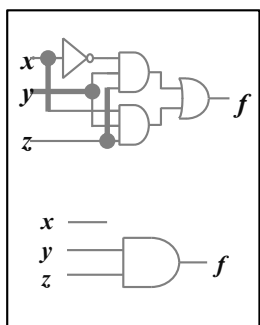

12

## MORE EXAMPLE IN TEXT BOOK

- See page 46.
- Example 2.7-2.9
- Hints:
  - Specification  $\Rightarrow$  Truth Table
  - Synthesize by means of Sum of Product
  - Simplify the expression in a number of ways

13

## CANONICAL FORMS – TERMINOLOGY

- Literal** – Any Boolean variable or its complement.  
Example:  $A, x, \bar{B}, \bar{x}, A+B$
- Sum Term** – Two or more literals joined by **OR** operators.  
Example:  $A+B+C, A+\bar{B}C$
- Product Term** – Two or more literals joined by **AND** operators.  
Example:  $ABC, \bar{x}y$
- Sum-of-Products** – two or more product terms or literals joined by **OR** operators.  
Example:  $A+\bar{B}C+\bar{B}D, A+B(C+D)$
- Product-of-Sums** – two or more sum terms or literals joined by **AND** operators.  
Example:  $A(\bar{B}+C)(\bar{B}+D), A(\bar{B}+CD)$

14

## CANONICAL FORMS – TERMINOLOGY (CON'D)

- Minterm** – a product term that contains each variable exactly once, in either complemented or uncomplemented form.  
Example:  $f$  is a Boolean function of the variables  $A, B, C, D$ .  
 $ABCD, \bar{A}BCD$
- Maxterm** – a sum term that contains each variable exactly once, in either complemented or uncomplemented form.  
Example:  $A+B+C+D, A+B+C+\bar{D}$
- Canonical Sum-of-Products** – A sum-of-products expression in which every product term is a minterm.  
Example:  $f(A,B,C,D) = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D}$   
 $f(A,B,C,D) = ABC + ABD$
- Canonical Product-of-sums** – A product-of-sums expression in which every sum term is a maxterm.  
Example:  $f(A,B,C,D) = (A+B+C+D)(\bar{A}+\bar{B}+C+D)(\bar{A}+\bar{B}+C+\bar{D})$   
 $f(A,B,C,D) = (A+B+C)(A+B+D)$

15

## RELATION IN CANONICAL FORMS

### Truth Tables:

- Suppose we have a truth table for a Boolean function of  $n$  variables. Let the rows be numbered 0 through  $2^n-1$ .
- Each row corresponds to one minterm. Let  $m_k$  be the minterm for row  $k$ . *It is the only minterm that is true for row  $k$ .*

Row	A	B
2	1	0

$$\Rightarrow m_2 = A\bar{B}$$

- Each row also corresponds to one maxterm. Let  $M_k$  be the maxterm for row  $k$ . *It is the only maxterm that is false for row  $k$ .*

Row	A	B
2	1	0

$$\Rightarrow M_2 = \bar{A}+B$$

16

## RELATION IN CANONICAL FORMS

- Example  $f(x, y, z)$

k	x	y	z
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

17

## MORE PROPERTIES OF MINTERM AND MAXTERM

- For  $n$  variable, there are  $(M = 2^n)$  maxterms or minterms and there are  $2^M$  possible logic expressions.
- For given value of variables, the product of more than two different Minterms is 0
- For given value of variables, the sum of more than two different Maxterms is 1
- Sum of all minterms for  $n$  variables is 1
- Product of all maxterms for  $n$  variables is 0
- Not  $m_i = M_i$

18

## CANONICAL SOP FORM

- 1) Write down the truth table for the logic function  $f$ .
- 2) For each row where  $f = 1$ , find the associated **minterm**.
- 3) The function  $f$  is the **sum of these minterms**.

**Example:** Prime number (smaller than 10) detector.

**Definition:** A prime number is an integer greater than 1 whose only divisors are 1 and itself.

**Goal:** Design a circuit to realize  $f(x,y,z)$  where  $f = 1$  if and only if  $xyz$  is a prime number.

19

## CANONICAL SOP FORM – EXAMPLE

### (1) Truth Table

$k$	$x$	$y$	$z$	$f$	$m_k$
0	0	0	0	0	$\bar{x}\bar{y}\bar{z}$
1	0	0	1	0	$\bar{x}\bar{y}z$
2	0	1	0	1	$\bar{x}y\bar{z}$
3	0	1	1	1	$\bar{x}yz$
4	1	0	0	0	$x\bar{y}\bar{z}$
5	1	0	1	1	$x\bar{y}z$
6	1	1	0	0	$xy\bar{z}$
7	1	1	1	1	$xyz$

### (2) Minterms

$$m_2 = \bar{x}y\bar{z}; \quad m_3 = \bar{x}yz; \quad m_5 = x\bar{y}z; \quad m_7 = xyz$$

### (3) Canonical SOP Expression


$$f = m_2 + m_3 + m_5 + m_7 = \sum m(2,3,5,7)$$

$$= \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}z + xyz$$

20

## CANONICAL SOP FORM – EXAMPLE

### (4) Logic Network

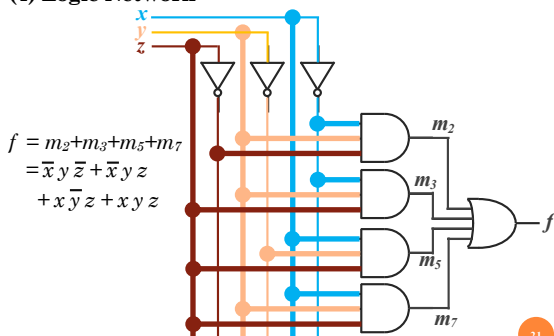

21

## CANONICAL POS FORM

- (a) Truth Table.
- (b) For each row where  $f = 0$ , find the associated **maxterms**.
- (c) The function  $f$  is the **product of these maxterms**.

Example: Prime Number (smaller than 10) Detector

22

## CANONICAL POS FORM – EXAMPLE

### (1) Truth Table

$k$	$x$	$y$	$z$	$f$	$m_k$	$M_k$
0	0	0	0	0	$\bar{x}\bar{y}\bar{z}$	$x+y+z$
1	0	0	1	0	$\bar{x}\bar{y}z$	$x+y+\bar{z}$
2	0	1	0	1	$\bar{x}y\bar{z}$	$x+\bar{y}+z$
3	0	1	1	1	$\bar{x}yz$	$x+\bar{y}+\bar{z}$
4	1	0	0	0	$x\bar{y}\bar{z}$	$\bar{x}+y+z$
5	1	0	1	1	$x\bar{y}z$	$\bar{x}+y+\bar{z}$
6	1	1	0	0	$xy\bar{z}$	$\bar{x}+\bar{y}+z$
7	1	1	1	1	$xyz$	$\bar{x}+\bar{y}+\bar{z}$

### (2) Maxterms

$$M_0 = x + y + z; \quad M_1 = x + y + \bar{z}; \quad M_4 = \bar{x} + y + z; \quad M_6 = \bar{x} + \bar{y} + z$$

### (3) Canonical POS Expression


$$f = M_0 \cdot M_1 \cdot M_4 \cdot M_6 = \prod M(0,1,4,6)$$

$$= (x + y + z) \cdot (x + y + \bar{z}) \cdot (\bar{x} + y + z) \cdot (\bar{x} + \bar{y} + z)$$

23

## CANONICAL POS FORM – EXAMPLE

### (4) Logic Network

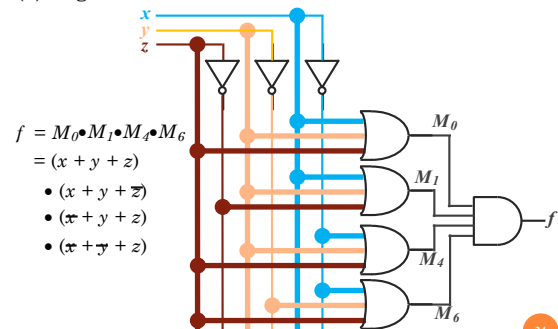

24

## EVALUATING A DESIGN


- Consider the **Prime Number Detector**...
  - Is this a good design?
  - Can we find a better one?
- Often the simplest design is best. For our purpose, we will try to minimize the following cost function:

$$\text{Cost} = \text{Total number of Gates} + \text{total number of Gate Inputs}$$

25

## EVALUATING A DESIGN
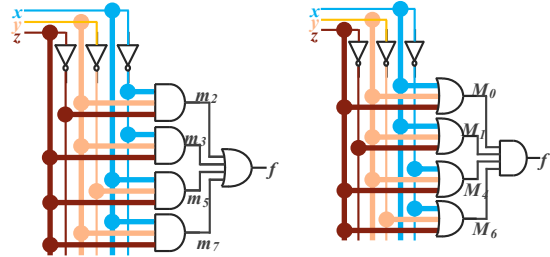
### Canonical SOP Network Canonical POS Network



26

## EVALUATING A DESIGN

### Canonical SOP Network Canonical POS Network

- |                                                                                                                                                                                |                                                                                                                                                                                |
|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <ul style="list-style-type: none"> <li>3 NOT Gates</li> <li>4 3-input AND Gates</li> <li>1 4-input OR Gates</li> <li>8 Gates, 19 Inputs</li> <li>Cost = 8 + 19 = 27</li> </ul> | <ul style="list-style-type: none"> <li>3 NOT Gates</li> <li>4 3-input OR Gates</li> <li>1 4-input AND Gates</li> <li>8 Gates, 19 Inputs</li> <li>Cost = 8 + 19 = 27</li> </ul> |
|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|

**Can we do better?**

27

## MINIMAL SOP REALIZATION

- Apply **postulates + theorems** of Boolean algebra to simplify expression as much as possible.
- Must remain in SOP form.

### Example:

$$\begin{aligned}
 f &= \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}z + xyz \\
 &= \bar{x}y(\bar{z} + z) + xz(\bar{y} + y) && \text{Distributive} \\
 &= \bar{x}y \cdot 1 + xz \cdot 1 && \text{Postulate 5a} \\
 &= \bar{x}y + xz && \text{Identity for } \cdot
 \end{aligned}$$




28

## MINIMAL POS REALIZATION

- Simplify expression.
- Must remain in POS form.
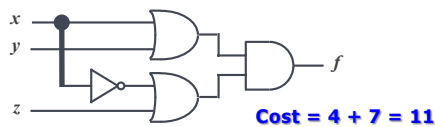
### Example:

$$\begin{aligned}
 f &= (x+y+z)(x+y+\bar{z})(\bar{x}+y+z)(\bar{x}+\bar{y}+z) \\
 &= (x+y+z \cdot \bar{z})(\bar{x}+z+y \cdot \bar{y}) && \text{Distributive} \\
 &= (x+y+0)(\bar{x}+z+0) && \text{Postulate 5a} \\
 &= (x+y)(\bar{x}+z) && \text{Identity for } +
 \end{aligned}$$



29

## Another Example for POS and SOP Realization

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

SOP:  
 $F = \sum m(1, 4, 5, 6)$

POS:  
 $F = \prod M(0, 2, 3, 7)$

Figure 2.23. A three-variable function.

30

## Then manipulation to reduce the cost

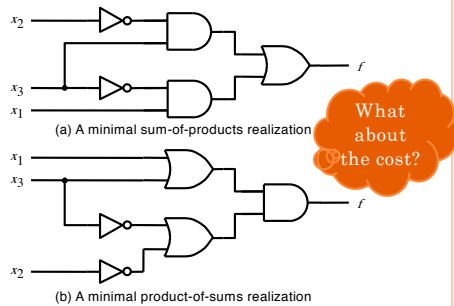


Figure 2.24. Two realizations of a function in Figure 2.23.

## More example in Textbook

- ▶ Example 2.10 shows how to simplify the SOP
- ▶ Example 2.11 also shows how to simplify the SOP
- ▶ Example 2.12 shows how to simplify the POS
- ▶ List the Useful identities
  - ▶  $AB + A\bar{B} = A$
  - ▶  $(A+B)(A+\bar{B}) = A$

## RELATION OF POS AND SOP

- SOP is an AND-OR network
- POS is an OR-AND network
- SOP and POS can be derived from each other
- For example:
  - Get the POS from the SOP
  - 1: Not F in the Truth Table
  - 2: Realize the Not F using SOP
  - 3: Not Not F to Get F and Simplify using the DeMorgan's theorem
  - Understand the identify : Not m = M


## CONCLUSION

- SOP/AND-OR network and POS/OR-AND network
- The general method to synthesize the function
- The relationship between SOP and POS
- Can calculate the cost

Cost: Page: 89 Chapter 2.12.1  
We will assume the input variables are available in both true and complemented forms at zero cost.

- Textbook Reading: Chapter 2.6, Pages:43-54
- Assignment: 2.10, 2.11, 2.12, 2.20, 2.22, 2.23

## 2.7 NAND AND NOR LOGIC NETWORKS

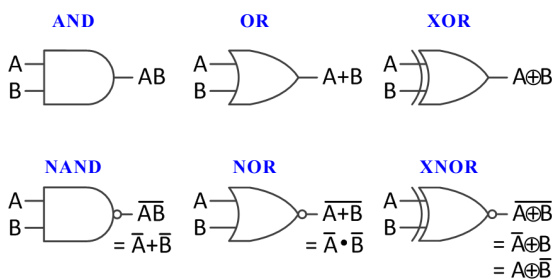

## DEMORGAN'S THEOREM IN TERMS OF LOGIC GATE



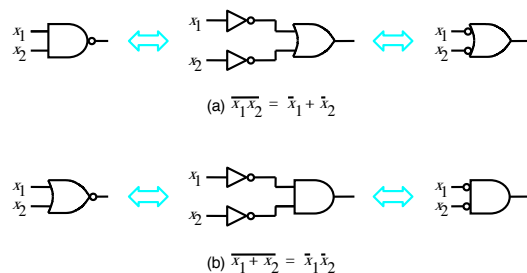
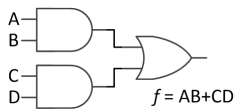


Figure 2.26. DeMorgan's theorem in terms of logic gates.

### SOP NETWORK

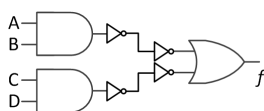

SOP Network  $\rightarrow$  All NAND

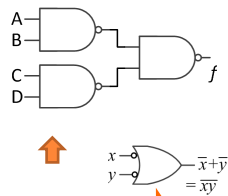


37


### NAND + NOR ARE UNIVERSAL

#### NAND


(i)  $\bar{A} = A \cdot \bar{A}$

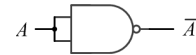

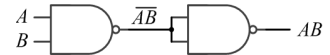(ii)  $A \cdot B = \overline{\overline{A \cdot B}}$



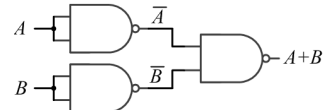(iii)  $A + B = \overline{\bar{A} \cdot \bar{B}}$



38


### NAND + NOR ARE UNIVERSAL

#### NOR


(i)  $\overline{A + A} = \bar{A}$



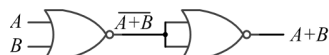(ii)  $\overline{\overline{A + B}} = A + B$





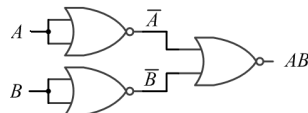(iii)  $\overline{\bar{A} + \bar{B}} = A \cdot B$




39
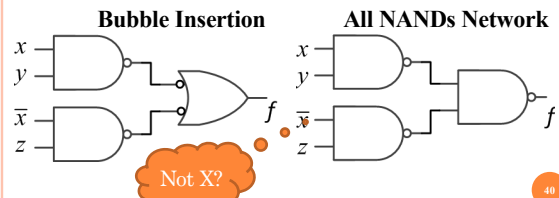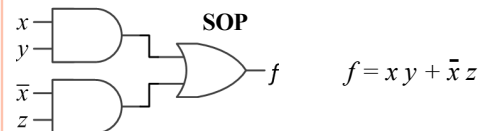
### Convert SOP network to ALL NANDs Network



40
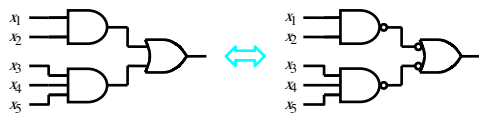
### CONVERT SOP NETWORK TO ALL NANDS NETWORK





Just has one kind of Gate

Figure 2.27. Using NAND gates to implement a sum-of-products.

41
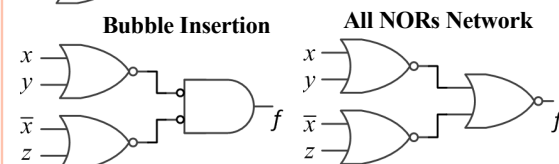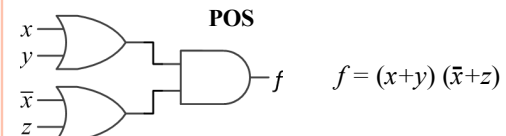
### Convert POS network to ALL NORs network



42

### CONVERT POS NETWORK TO **ALL NOR** NETWORK

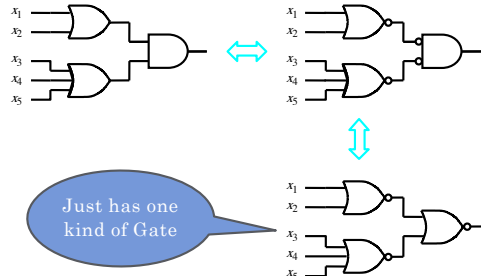


Figure 2.28. Using NOR gates to implement a product-of sums.

### EXAMPLE IN THE TEXTBOOK

- Example 2.13
- Implement the function  $F(x_1, x_2, x_3) = \sum m(2, 3, 4, 6, 7)$  using NOR gates only.
- Ans:  $F = (x_1 + x_2)(x_2 + \bar{x}_3)$
- Example 2.14
- Implement the above function using the NAND gates only
- Ans:  $F = x_2 + x_1 \bar{x}_3$

### LOGIC CIRCUIT USING NAND AND NOR

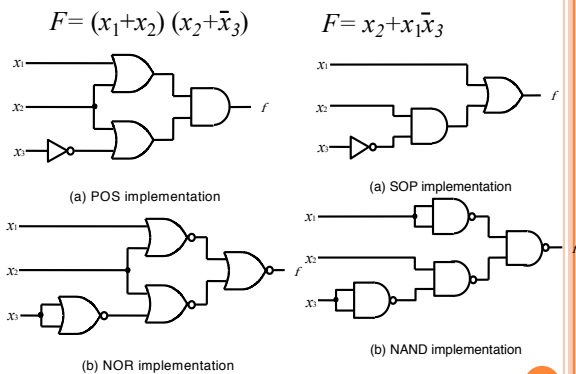


Figure 2.29 NOR-gate realization Figure 2.30. NAND-gate realization

### TWO QUESTIONS?

- Why do we need the NAND or NOR Network?
  - Because simple transistor circuit
  - Show the transistor model
- Can we directly derive the logic expression of NOR/NAND network
  - Yes  $F = \text{NOT}(\text{NOT } F)$
  - Example  $F = AB + CD = AB \cdot CD$

### CONCLUSION

- NAND Logic networks
- NOR Logic networks
- Can solve simple problem to Circuit

- Textbook Reading: Chapter 2.7, Pages:54-59
- Assignment: 2.28, 2.31, 2.35

### 2.8 DESIGN EXAMPLES

#### (1) Three-way light control

Assume that a large room has three doors and that a switch near each door controls a light in the room. It has to be possible to turn the light on or off by changing the state of any one of the switches.



### THREE-WAY LIGHT CONTROL

#### ○ A. Truth table

$x_1$	$x_2$	$x_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Figure 2.31. Truth table for a three-way light control.

49

### THREE-WAY LIGHT CONTROL

#### ○ B. The canonical function

##### ○ sum-of-products form

$$f = m_1 + m_2 + m_4 + m_7$$

$$= x_1 \bar{x}_2 x_3 + \bar{x}_1 x_2 \bar{x}_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 x_3$$

##### ○ product-of-sums form

$$f = M_0 \cdot M_3 \cdot M_5 \cdot M_6$$

$$= (x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + x_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + x_3)$$


$x_1$	$x_2$	$x_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

50

### THREE-WAY LIGHT CONTROL
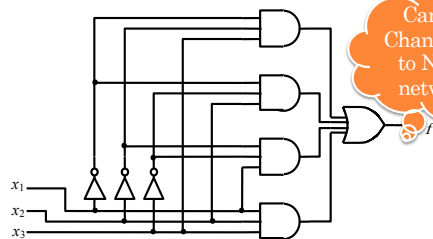
#### ○ C. SOP realization

$$f = x_1 x_2 x_3 + \bar{x}_1 x_2 \bar{x}_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 \bar{x}_3$$



(a) Sum-of-products realization


Figure 2.32. Implementation of the function in Figure 2.31.

51

### THREE-WAY LIGHT CONTROL
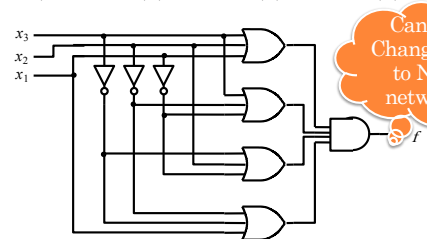
#### ○ C. POS realization

$$f = (x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + x_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + x_3)$$



(b) Product-of-sums realization

Figure 2.32. Implementation of the function in Figure 2.31.

52

### MULTIPLEXER CIRCUIT

#### ○ (2) Multiplexer circuit

Suppose that there are two sources of data, provided as input signals  $x_1$  and  $x_2$ .

We want to design a circuit that produces an output that has the same value as either  $x_1$  or  $x_2$ , dependent on the value of a selection control signal  $s$ .

Therefore, the circuit should have three inputs:  $x_1$ ,  $x_2$ , and  $s$ .

Assume that the output of the circuit will be the same as the value of input  $x_1$  if  $s=0$ , and it will be the same as  $x_2$  if  $s=1$ .

53

### MULTIPLEXER CIRCUIT

#### ○ A. Truth table

$s$	$x_1$	$x_2$	$f(s, x_1, x_2)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

(a) Truth table


#### ○ B. The canonical function

$$f = \bar{s}x_1 + sx_2$$

54

## MULTIPLEXER CIRCUIT

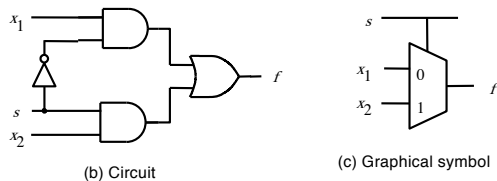- C. Circuit realization:  $f = \bar{s}x_1 + sx_2$



(d) More compact truth-table representation

s	$f(s, x_1, x_2)$
0	$x_1$
1	$x_2$


55

## EXTENSION OF MULTIPLEXER

- 4-to-1
- 8-to-1

56

## NUMBER DISPLAY

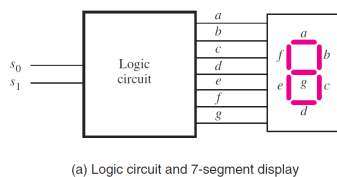

(a) Logic circuit and 7-segment display

(b) Truth table

$s_1$	$s_0$	a	b	c	d	e	f	g
0	0	1	1	1	1	1	1	0
0	1	0	1	1	0	0	0	0
1	0	1	1	0	1	1	0	1

$a = d = e = \bar{s}_0$   
 $b = 1$   
 $c = \bar{s}_1$   
 $f = \bar{s}_1 \bar{s}_0$   
 $g = s_1 \bar{s}_0$

Figure 2.34. Display of numbers.

57

- Problems: For the timing diagram in Figure p2.3, synthesize the function  $f(x_1, x_2, x_3)$  in the simplest sum-of-products form.

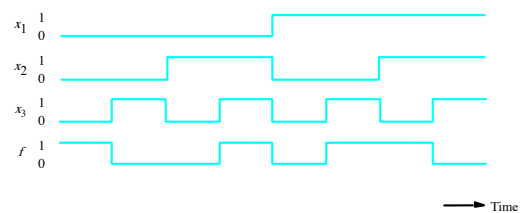


Figure p2.3. A timing diagram representing a logic function.

58

## CONCLUSION

- Can solve simple problem to Circuit
- Textbook Reading: Chapter 2.8, Pages:59-64
- Assignment: 2.51, 2.52, 2.54, 2.56

59